

DIGITAL CIRCUITS

LECTURE 06-1

JIM FIX, REED COLLEGE CS2-F20

WHERE WE ARE AT IN THE SCHEDULE

- ▶ **TODAY:** Part II. Circuits and Processors.
 - Download **Logisim-Evolution** for simulating digital circuits.
 - Needs installation of Oracle's **JDK** (Java Development kit) or of **OpenJDK**

RANDOM FACT ABOUT MY PROGRAMMING HISTORY


- ▶ I had a summer internship worked on a full-scale nuclear reactor simulator.
- ▶ I was asked to transcribe logic circuits into FORTRAN code.
- ▶ There were reactor control diagrams for control behavior, e.g.

If that valve has not failed and that pipe's pressure is normal, or we are in shutdown mode, then a certain green light on the control panel should be lit up.

- ▶ That logic might lead to this code in C++:



```
bool v = valve_failure(vlv120);  
bool p = pressure_normal(ps456);  
bool s = in_shutdown_mode(system);  
g = (!v && p) || s
```

BEHAVIOR WAS ENCODED AS A RELAY CIRCUIT

 

TRANSISTOR LOGIC

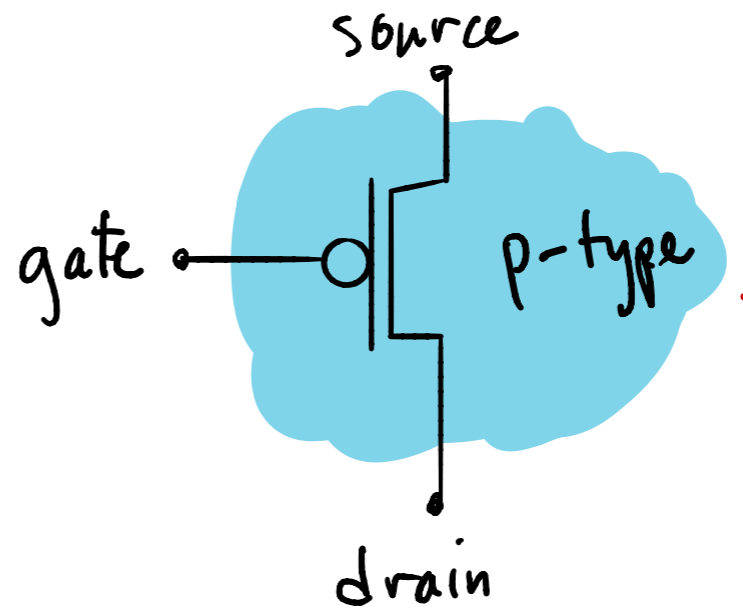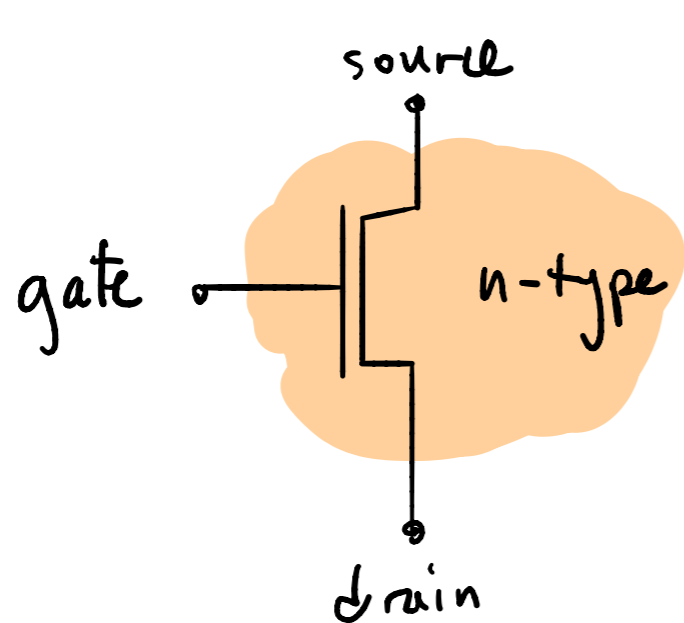
There are two kinds of transistors: n-type and p-type



- gate/source/drain wired up possibly to HIGH/Low voltage (e.g. +5V/+0V)
- pathway between source-drain "gated", acts like a switch controlled by gate signal

TRANSISTOR LOGIC


n-type transistor behavior

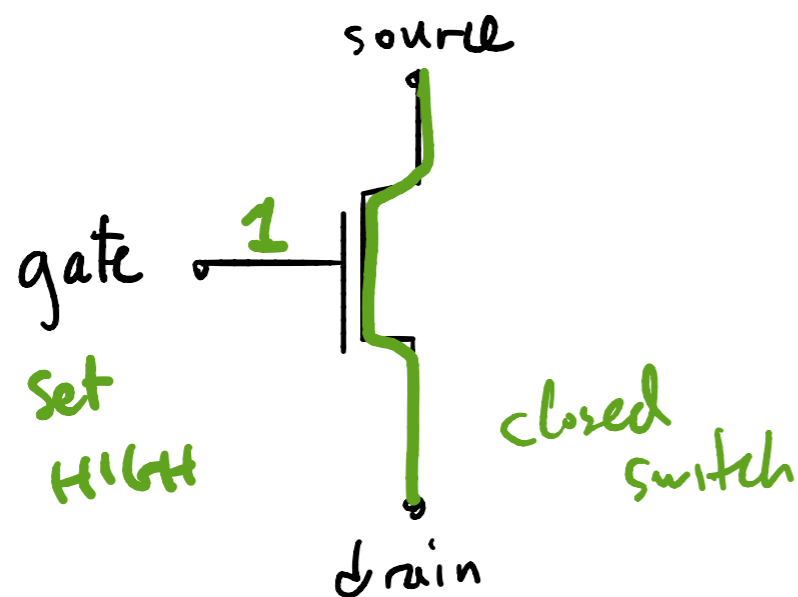


⇒ When an n-type transistor's gate is connected HIGH (signal of "1") it acts like a closed switch from the source to the drain.

TRANSISTOR LOGIC

n-type transistor behavior

 


 
⇒ When an n-type transistor's gate is connected to HIGH (signal of "1") it acts like a closed switch from the source to the drain.



⇒ when its gate is connected to Low (set "0") it acts like an open switch. Does not conduct.

TRANSISTOR LOGIC

p-type transistor behaves oppositely...

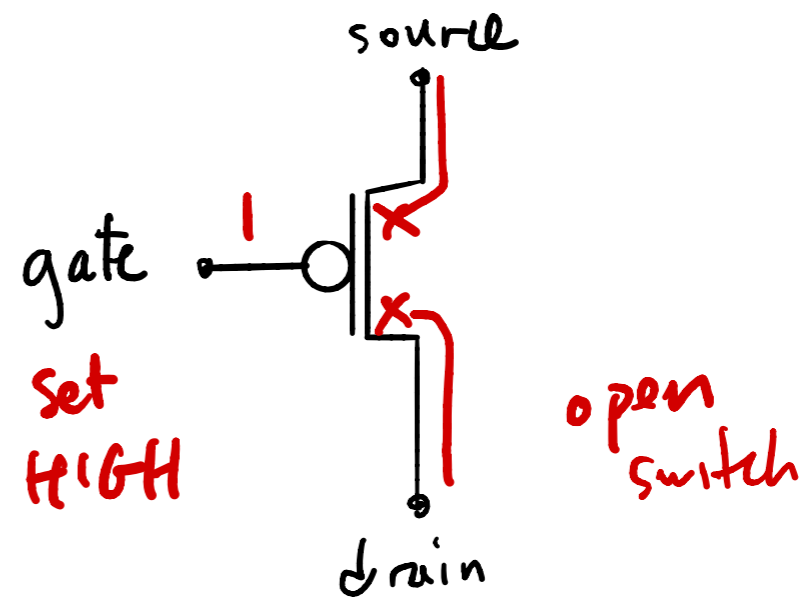
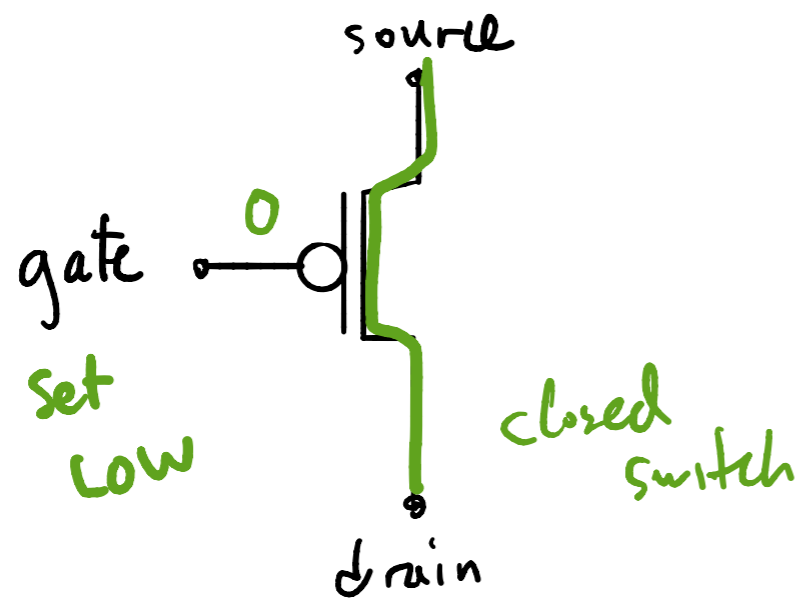


Its logic is inverted...
⇒ when gate is Low (0)
the p-type transistor conducts.

⇒ when gate is set HIGH (1)
it does not conduct.

TRANSISTOR LOGIC

Summary:

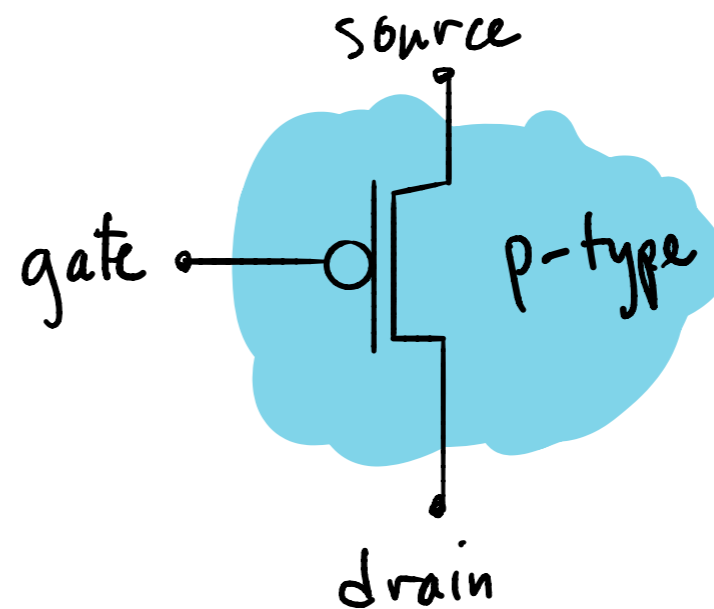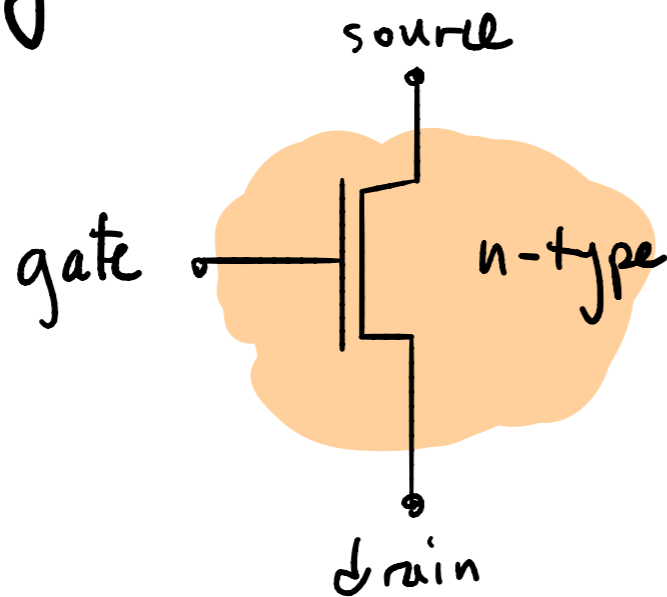


n-type

- when gate connected to HIGH, conduction between source and drain
- when connected to LOW, no conduction

p-type

- when gate connected to LOW, conduction between source and drain
- when connected to HIGH, no conduction

TRANSISTOR LOGIC: INVERTER

 


How does this transistor circuit behave?

truth table:

X	output
Low	??
HIGH	??

TRANSISTOR LOGIC: INVERTER

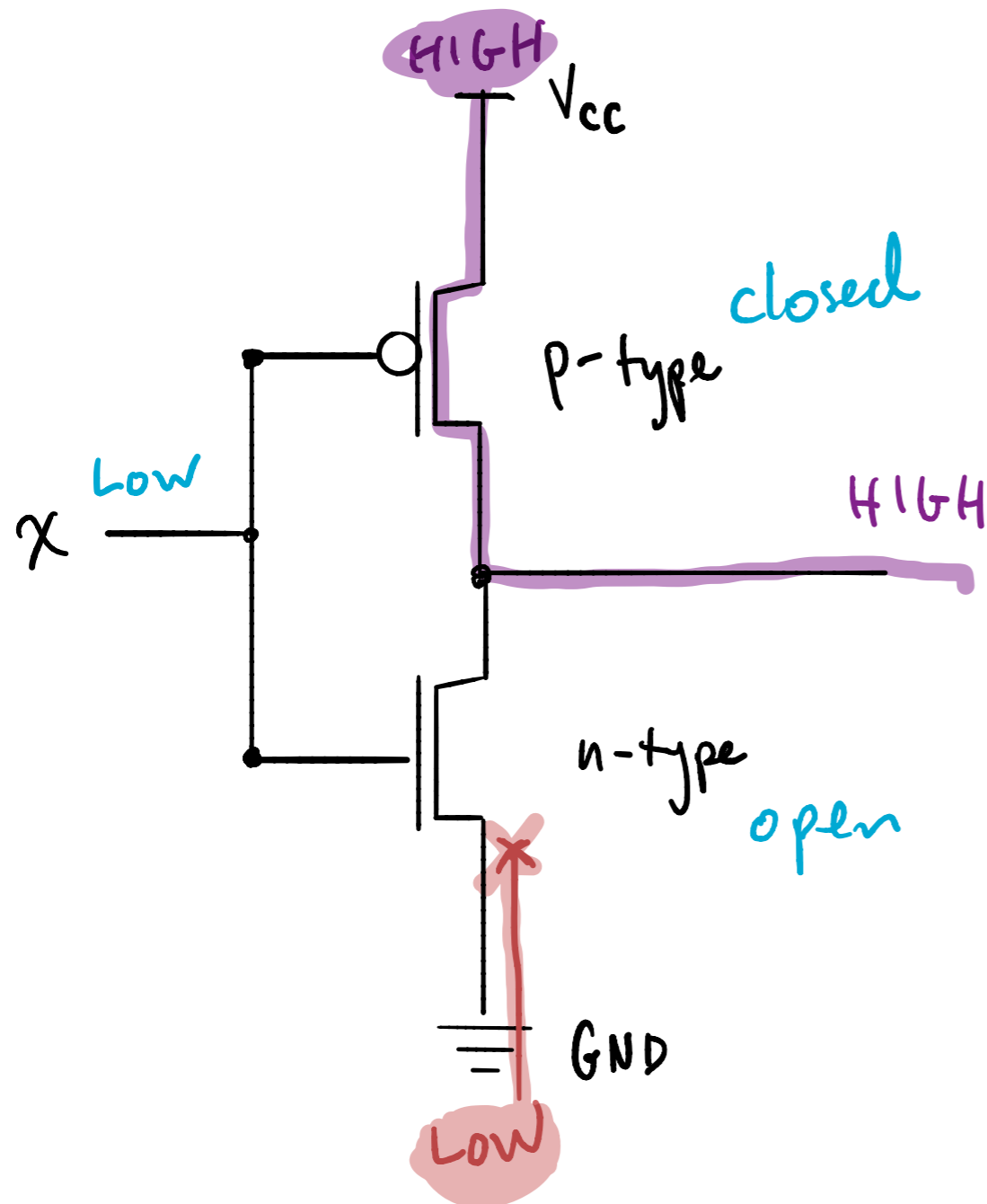

Let's set the input line x to LOW...


truth table:

⇒

x	output
Low	HIGH
HIGH	

⇐

TRANSISTOR LOGIC: INVERTER

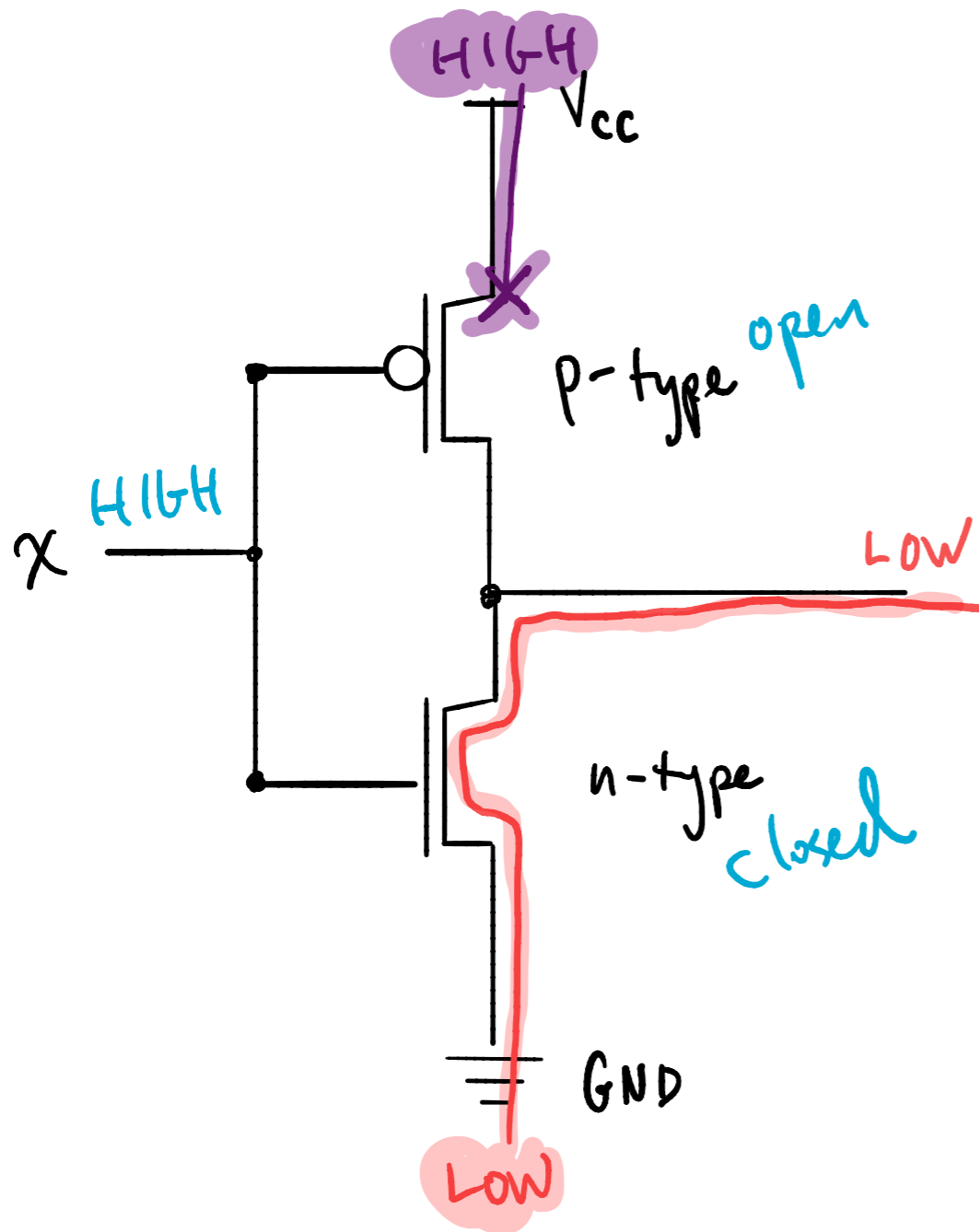


let's set the input line x to HIGH...

truth table:

x	output
Low	HIGH
HIGH	Low


⇒

TRANSISTOR LOGIC: INVERTER

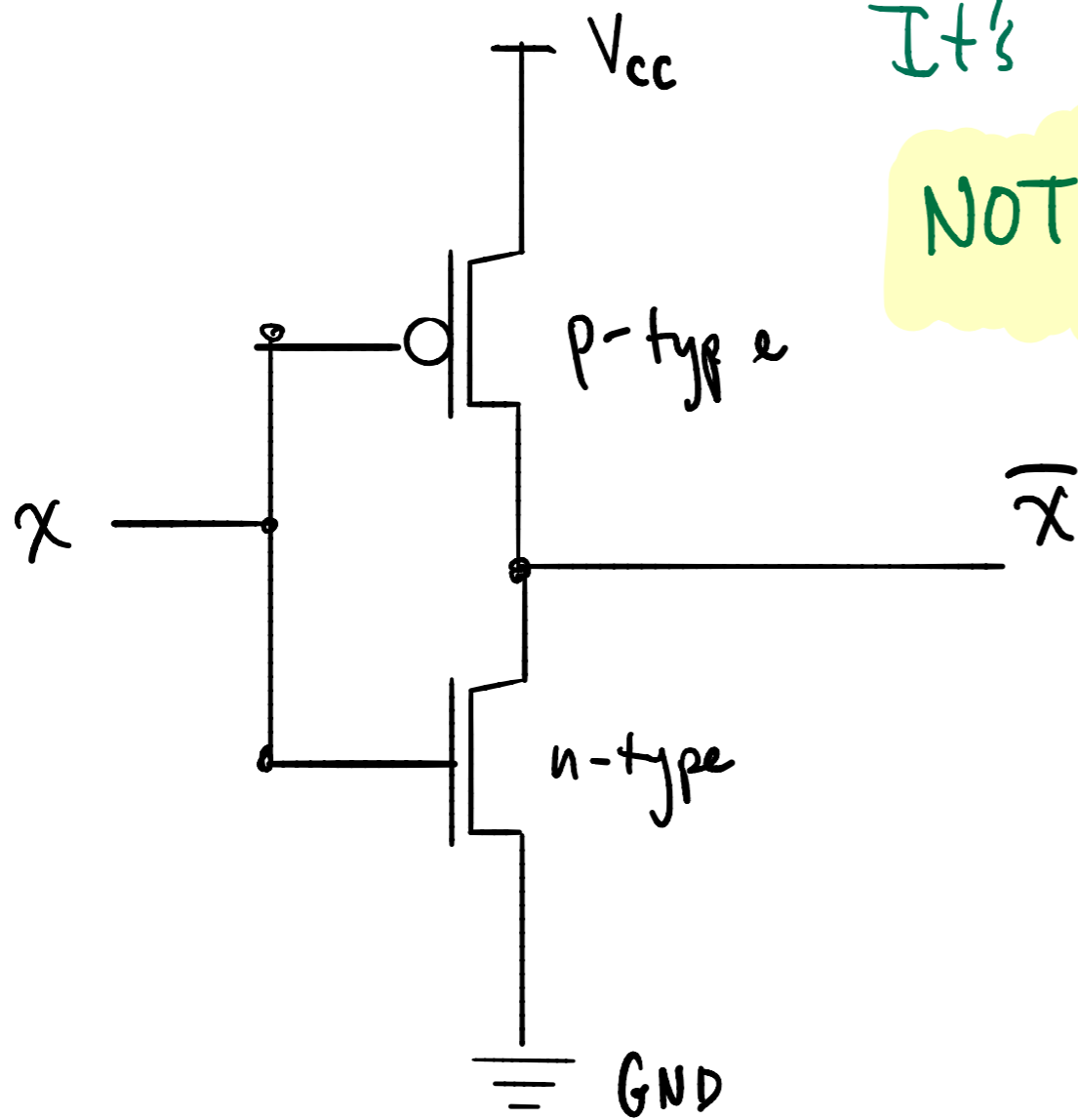

It's a
NOT gate!


Symbol:

 


truth table:

x	\bar{x}
0	1
1	0

TRANSISTOR LOGIC: OR GATE

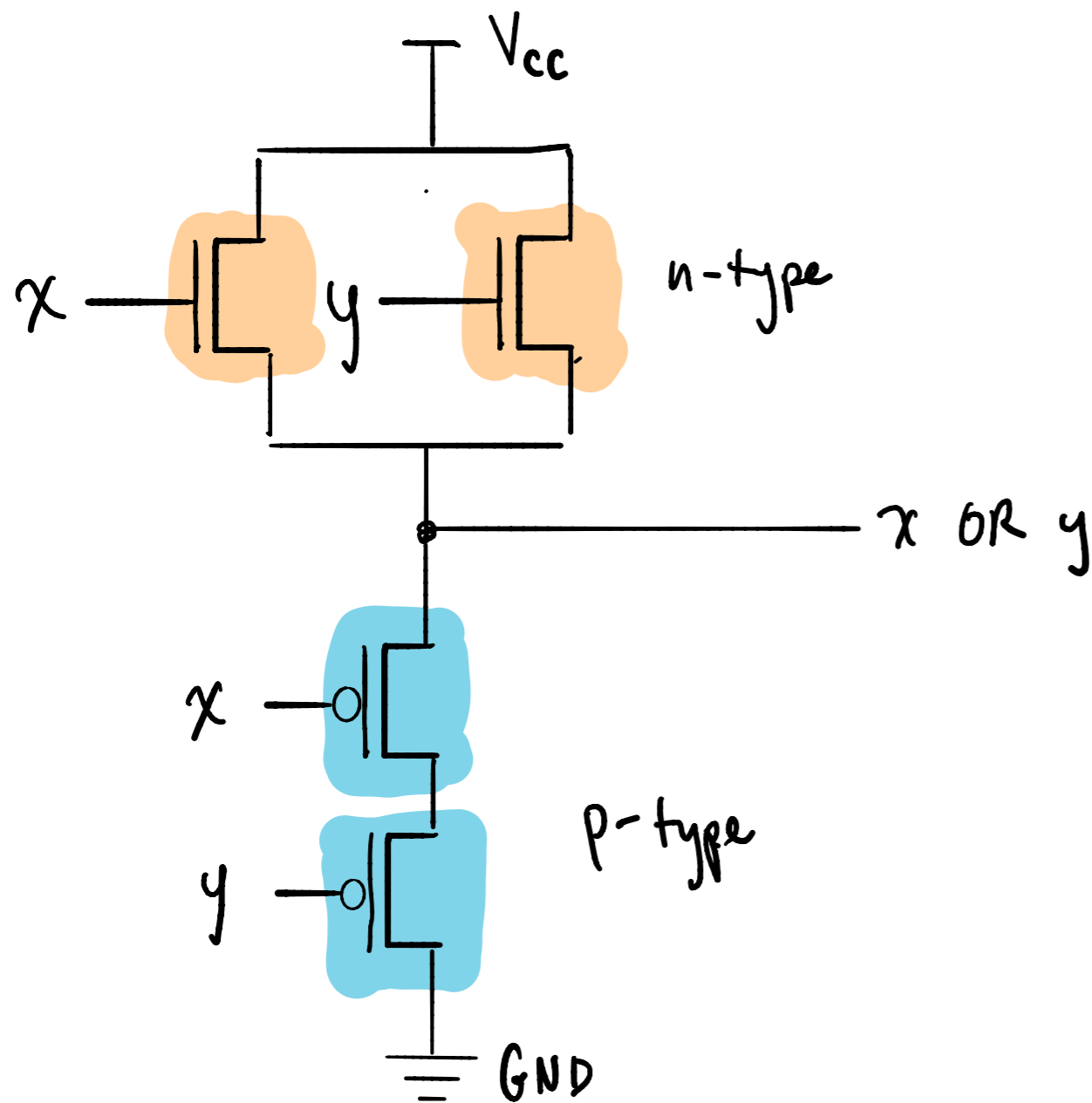


Symbol:

 


truth table:

x	y	$x \text{ OR } y$
Low	Low	Low
Low	HIGH	HIGH
HIGH	Low	HIGH
HIGH	HIGH	HIGH

TRANSISTOR LOGIC: OR GATE

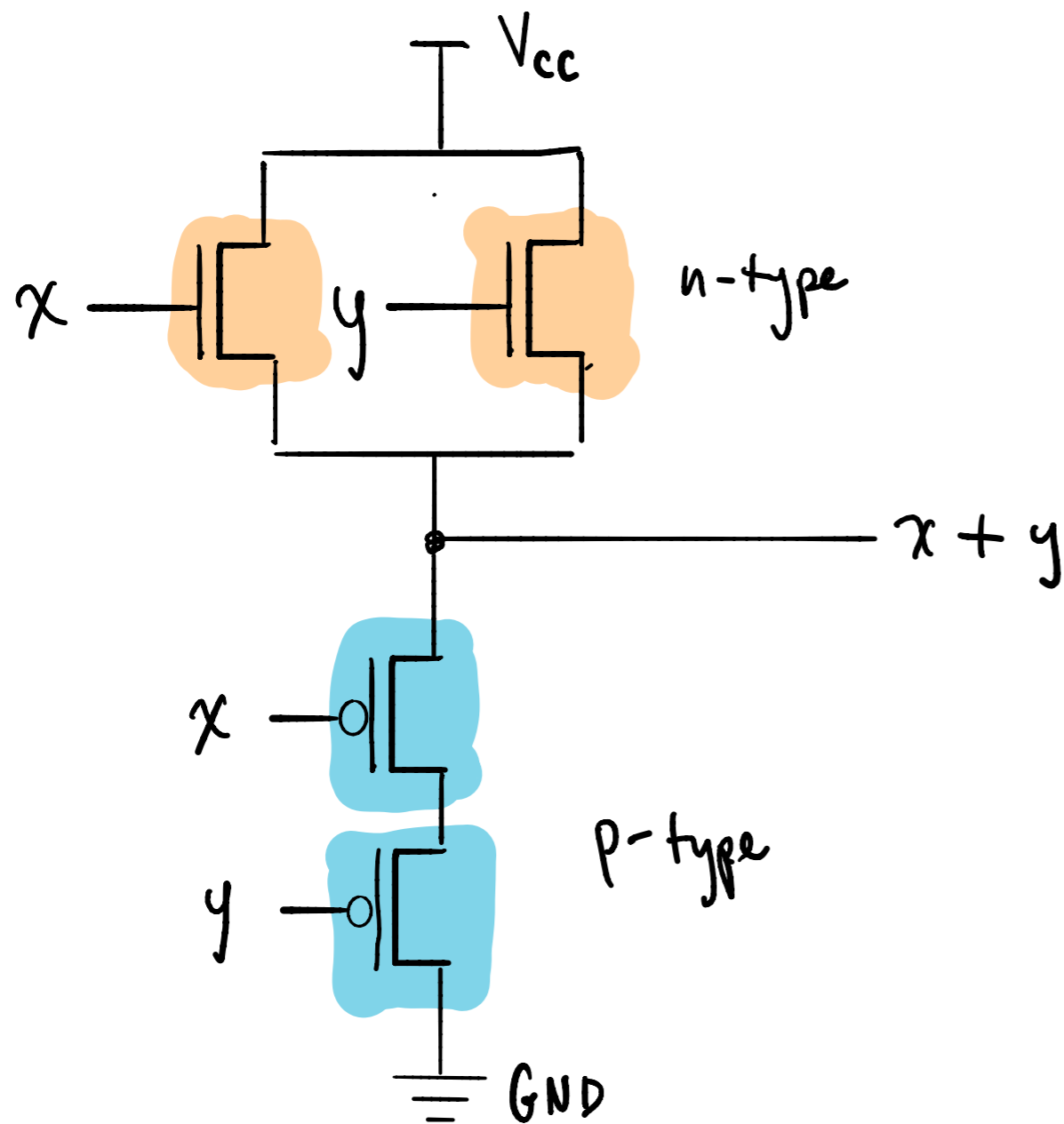


Symbol:

 


truth table:

x	y	$x + y$
0	0	0
0	1	1
1	0	1
1	1	1

TRANSISTOR LOGIC: AND GATE

 


Symbol:

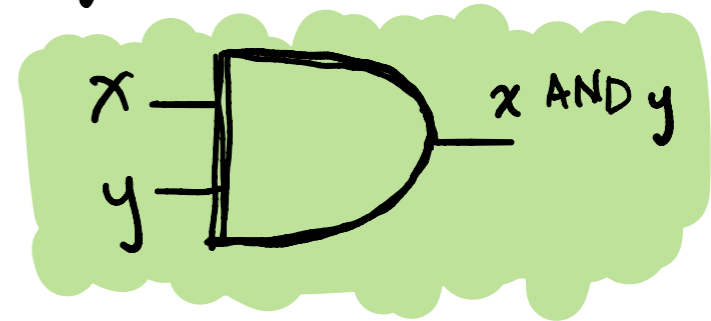


truth table:

x	y	$x \text{ AND } y$
Low	Low	Low
Low	HIGH	Low
HIGH	Low	Low
HIGH	HIGH	HIGH

TRANSISTOR LOGIC: AND GATE

 


Symbol:

 

truth table:

x	y	$x \cdot y$
0	0	0
0	1	0
1	0	0
1	1	1

REACTOR CONTROL CIRCUIT

 

Boolean expression:

$((\text{NOT } v) \text{ AND } p) \text{ OR } s$ "pythonic"

$((!v) \&\& p) || s$ C++


$(\neg v \wedge p) \vee s$ CS theory

$v \cdot p + s$ digital design

truth table

v	p	s	g
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

REACTOR CONTROL CIRCUIT

 

$$g := ((\text{NOT } v) \text{ AND } p) \text{ OR } s$$

Alternatively...

$$g := \bar{v} \cdot p + s$$

truth table

v	p	s	g
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

EXCLUSIVE OR CIRCUIT

- logical OR is inclusive
true when both inputs
true or either is true

inclusive OR t.t.

x	y	$x + y$
0	0	0
0	1	1
1	0	1
1	1	1

- exclusive OR
true when exactly
one input is true

exclusive OR t.t.

x	y	$x \oplus y$
0	0	0
0	1	1
1	0	1
1	1	0

EXCLUSIVE OR CIRCUIT

Let's express the logic of XOR using AND, OR, NOT, ...

exclusive OR t.t.

x	y	$x \oplus y$
0	0	0
0	1	1
1	0	1
1	1	0

Consider rows where output is one. Describe their input configuration...

2nd row: $\bar{x} \cdot y$

EXCLUSIVE OR CIRCUIT

Let's express the logic of XOR using AND, OR, NOT, ...

exclusive OR t.t.

x	y	$x \oplus y$
0	0	0
0	1	1
1	0	1
1	1	0

Consider rows where output is one. Describe their input configuration...

2nd row: $\bar{x} \cdot y$

3rd row: $x \cdot \bar{y}$

EXCLUSIVE OR CIRCUIT

Let's express the logic of XOR using AND, OR, NOT, ...

exclusive OR t.t.


x	y	$x \oplus y$
0	0	0
0	1	1
1	0	1
1	1	0

Boolean expression is just inclusive or of those cases...


$$\bar{x} \cdot y + x \cdot \bar{y}$$

This method always yields a sum of products.

EXCLUSIVE OR CIRCUIT

 

symbol:

 


truth table:

x	y	$x \oplus y$
0	0	0
0	1	1
1	0	1
1	1	0


$$x \oplus y := \bar{x} \cdot y + x \cdot \bar{y}$$

EXCLUSIVE OR CIRCUIT

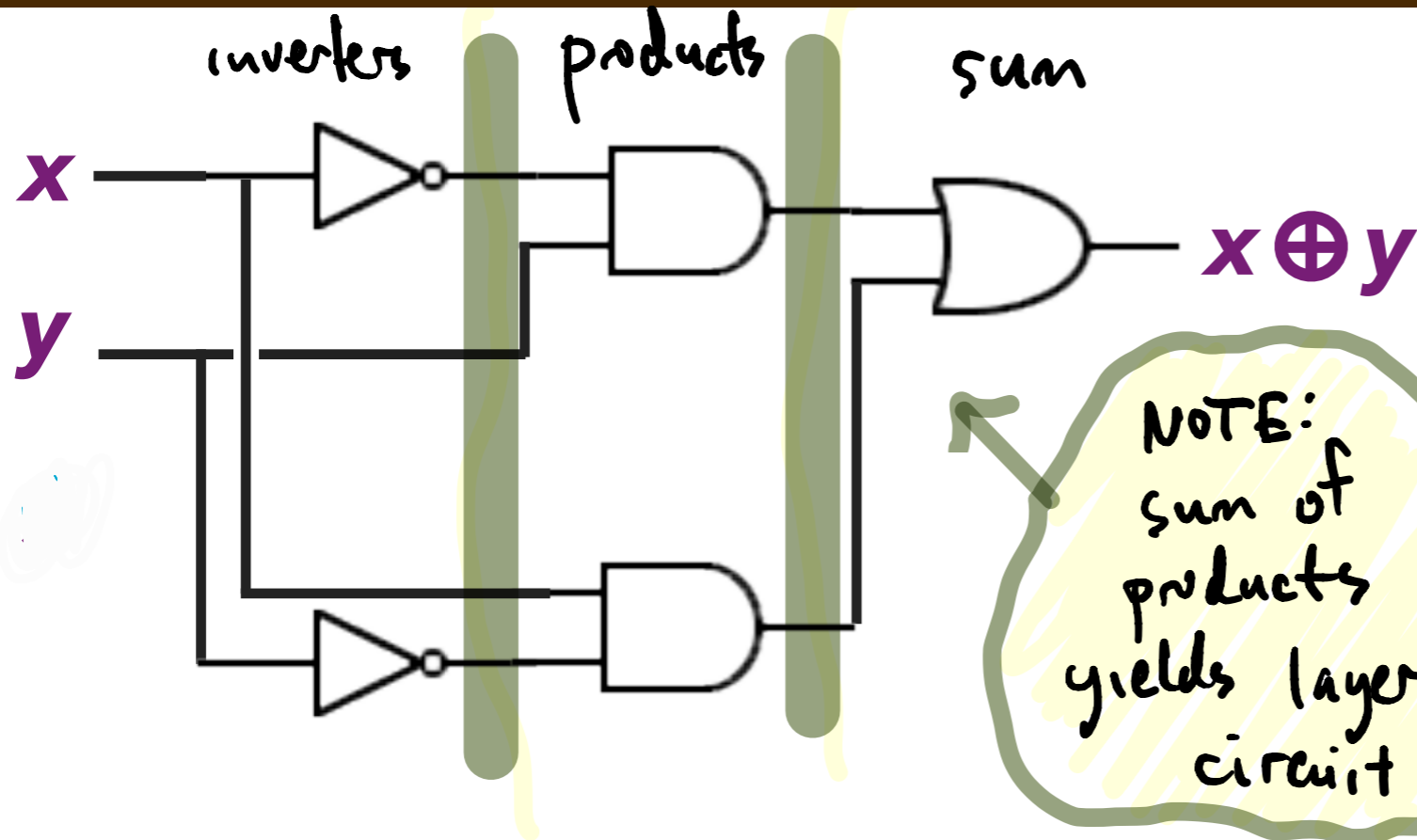

NOTE:
sum of
products
yields layered
circuit

symbol:

 

truth table:

x	y	$x \oplus y$
0	0	0
0	1	1
1	0	1
1	1	0

$$x \oplus y := \bar{x} \cdot y + x \cdot \bar{y}$$

In various boolean expression notations...

$$((\text{NOT } x) \text{ AND } y) \text{ OR } (x \text{ AND } (\text{NOT } y))$$


$$((!x) \& \& y) \parallel (x \& \& (!y))$$

$$((\neg x) \wedge y) \vee (x \wedge (\neg y))$$

$$\bar{x} \cdot y + x \cdot \bar{y}$$

2:1 MULTIPLEXER CIRCUIT

Can create a "switch-like circuit":

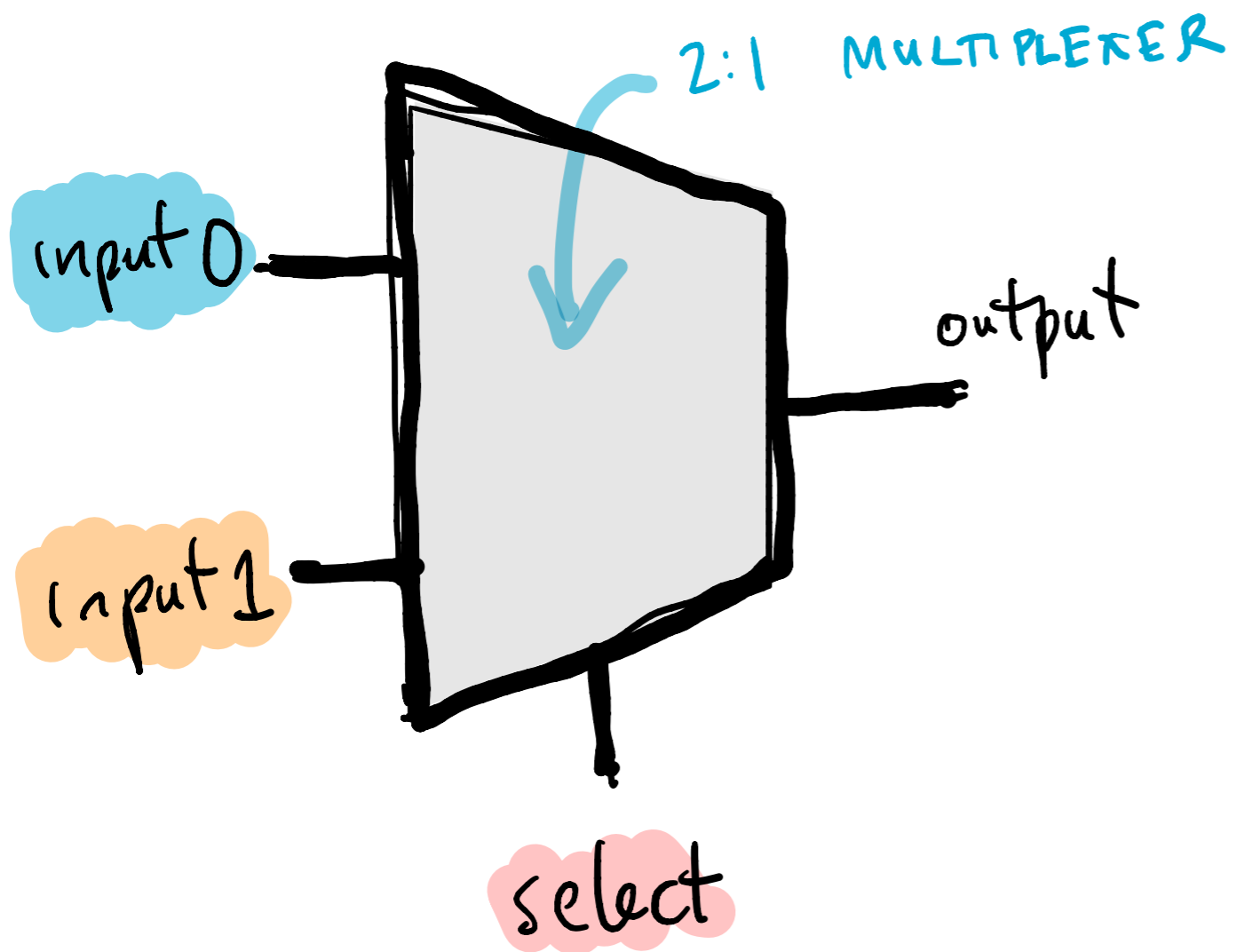


S	i_0	i_1	o
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

2.1 MULTIPLEXER CIRCUIT

Can create a "switch-like circuit":

With select set to 0, outputs input 0...

 


S	i_0	i_1	o
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

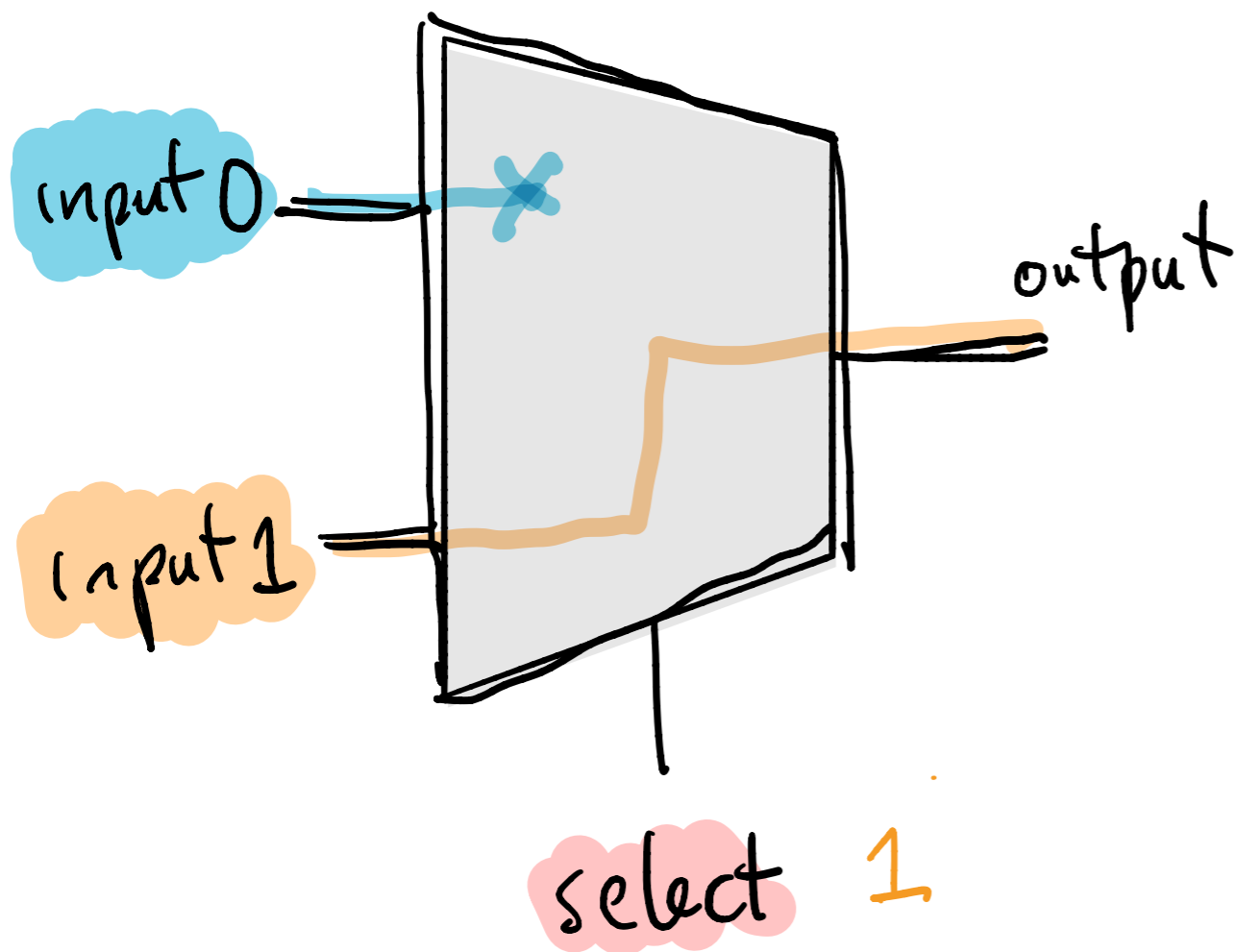2.1 MULTIPLEXER CIRCUIT


Can create a "switch-like circuit":

With select set to 1, outputs input 1 ...



S	i_0	i_1	o
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

2.1 MULTIPLEXER CIRCUIT

 

S	i_0	i_1	o
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

2.1 MULTIPLEXER CIRCUIT

Let's express the logic using AND, OR, NOT...

$$\theta := \begin{aligned} & \bar{S} \cdot i_0 \cdot \bar{i}_1 \quad \leftarrow \text{green arrow} \\ & + \\ & \bar{S} \cdot i_0 \cdot i_1 \quad \leftarrow \text{blue arrow} \\ & + \\ & S \cdot \bar{i}_0 \cdot i_2 \quad \leftarrow \text{purple arrow} \\ & + \\ & S \cdot i_0 \cdot i_1 \quad \leftarrow \text{red arrow} \end{aligned}$$

S	i_0	i_1	θ
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

The table shows the truth table for the multiplexer output θ . The input variables are S , i_0 , and i_1 . The output θ is 1 for the input combinations (0,1,0), (0,1,1), (1,0,1), and (1,1,1), and 0 otherwise. Colored circles and arrows next to the output column indicate the corresponding minterms from the logic expression: green for (0,1,0), blue for (0,1,1), purple for (1,0,1), and red for (1,1,1).

2.1 MULTIPLEXER CIRCUIT

Let's express the logic using AND, OR, NOT...


$$\theta := \left\{ \begin{array}{l} \bar{s} \cdot i_0 \cdot \bar{i}_1 + \bar{s} \cdot i_0 \cdot i_1 \\ + \\ s \cdot \bar{i}_0 \cdot i_1 + s \cdot i_0 \cdot i_1 \end{array} \right\} = \begin{array}{l} \bar{s} \cdot i_0 \\ + \\ s \cdot i_1 \end{array}$$

see below
similar


Note that:

$$\bar{s} \cdot i_0 \cdot \bar{i}_1 + \bar{s} \cdot i_0 \cdot i_1 = \bar{s} \cdot i_0 (\bar{i}_1 + i_1) = \bar{s} \cdot i_0 \cdot 1 = \bar{s} \cdot i_0$$

2.1 MULTIPLEXER CIRCUIT

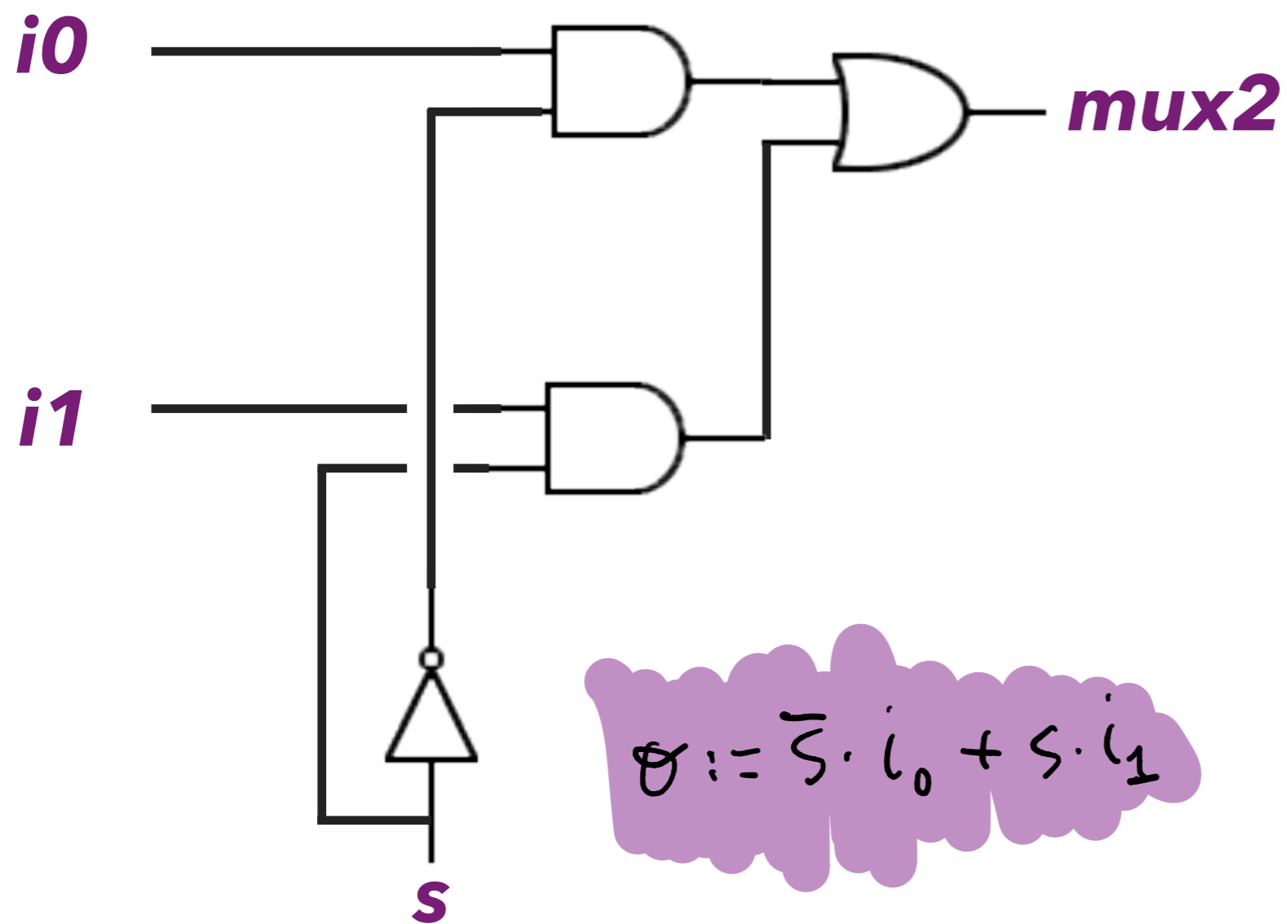

Symbol:

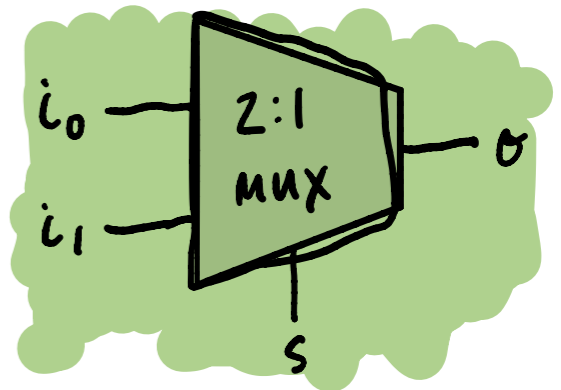

truth table:

s	i_0	i_1	o
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

We'll look at some more boolean algebra rules on Wednesday...

We'll also use MUX ad adders to build a calculator circuit.